

# CS5110: Complexity Theory

Shreyas Havaladar  
CS18BTECH11042

November 10, 2020

## 1 Exercise Set 13, Lecture 18

### 1.1 Solving Recurrence for Size

$$f(n) = 2f(\sqrt{n}) + 2\sqrt{n} + 1$$

Replacing  $n$  by  $2^k$  throughout

$$f(2^k) = 2f\left(2^{\frac{k}{2}}\right) + 2\sqrt{2^k} + 1$$

$$\implies f(2^k) = 2f\left(2^{\frac{k}{2}}\right) + 2^{\frac{k}{2}+1} + 1$$

To simplify our analysis. now let:  $T(k) = f(2^k)$

$$\implies T(k) = 2T\left(\frac{k}{2}\right) + 2^{\frac{k}{2}+1} + 1$$

Now looking at the Master Theorem stated below.

#### The Master Theorem

$$T(n) = \begin{cases} c & \text{if } n < d, \\ aT\left(\frac{n}{b}\right) + f(n) & \text{if } n \geq d, \end{cases}$$

where  $a \geq 1, b > 1$ , and  $d$  are integers and  $c$  is a positive constant.

- Case (i)  $f(n) = O(n^{\log_b a - \epsilon})$  for some  $\epsilon > 0$ :  $T(n) = \Theta(n^{\log_b a})$
- Case (ii)  $f(n) = \Theta(n^{\log_b a})$ :  $T(n) = \Theta((n^{\log_b a}) \cdot \log n)$
- Case (iii)  $f(n) = \Omega(n^{\log_b a + \epsilon})$  for some  $\epsilon > 0$  and  $af\left(\frac{n}{b}\right) \leq cf(n)$  for some  $c < 1$  for large enough  $n$ :  $T(n) = \Theta(f(n))$

So in our recurrence relation for  $T(n)$ , our  $a = 2, b = 2$ , thus  $n^{\log_b a} = n$ , and  $f(n)$  is clearly  $O(n^{\log_b a + \epsilon})$  for some  $\epsilon$ , as our  $f(n) = 2^{\frac{n}{2}+1} + 1$ , which is exponential and thus Case (iii) of The Master Theorem can be applied and we get, on re-substituting  $k$  as  $\log n$ , throughout the expression.

$$T(n) = \Theta(f(n))$$

$$\implies \boxed{T(n) = \Theta(\sqrt{n})}$$

**Note for number of wires:** We would solve the recursion relation for number of wires in the same manner. Only difference would be in  $f(n) = 2^{n+1} + 2$  as shown below. And we again would apply Master Theorem and as Case 3 condition is satisfied again as  $a$  and  $b$  values are same just the  $f(n)$  differs,  $T(n) = \Theta(n)$  on re-substituting  $k$  as  $\log n$  in  $f(k)$ . The bound remains the same on solving recursively so no advantage over the result we found in class by doing brute-force.

$$f(n) = 2f(\sqrt{n}) + 2n + 2$$

Replacing  $n$  by  $2^k$  throughout

$$f(2^k) = 2f\left(2^{\frac{k}{2}}\right) + 2 \cdot 2^k + 2$$

$$\implies f(2^k) = 2f\left(2^{\frac{k}{2}}\right) + 2^{k+1} + 2$$

To simplify our analysis. now let:  $T(k) = f(2^k)$

$$\implies T(k) = 2T\left(\frac{k}{2}\right) + 2^{k+1} + 2$$

So in our recurrence relation for  $T(n)$ , our  $a = 2, b = 2$ , thus  $n^{\log_b a} = n$ , and  $f(n)$  is clearly  $O(n^{\log_b a + \epsilon})$  for some  $\epsilon$ , as our  $f(n) = 2^{n+1} + 2$ , which is exponential and thus Case (iii) of The Master Theorem can be applied and we get, on re-substituting  $k$  as  $\log n$ , throughout the expression.

$$T(n) = \Theta(f(n))$$

$$\implies \boxed{T(n) = \Theta(n)}$$

## 1.2

Please look at the circuit on the next page.

**Size:** (2 OR gates for each  $\log n$  divisions into two buckets, for  $\log n$  bit positions, one each for each bucket) + ( $\log n$  AND gates corresponding to each  $F$ , to combine the outputs of the 2 OR gates corresponding to each bucket a level below) + (One topmost OR gate to combine the results of all  $\log n$  AND gates corresponding to each  $F$ )

$$Size = 2 \log n + \log n + 1$$

$$= 3 \log n + 1$$

$$= \boxed{O(\log n)}$$

**Number of Wires:** ( $2 * (n/2)$  wires, one each for each variable as input to the OR gate corresponding to each bucket, both of size  $(n/2)$  as with equal number of numbers with 1 at a position  $k$  and 0 at the position  $k$ )\*(Total lowermost OR gates which are  $\log n$ ) + (2 inputs per  $\log n$  AND gates corresponding

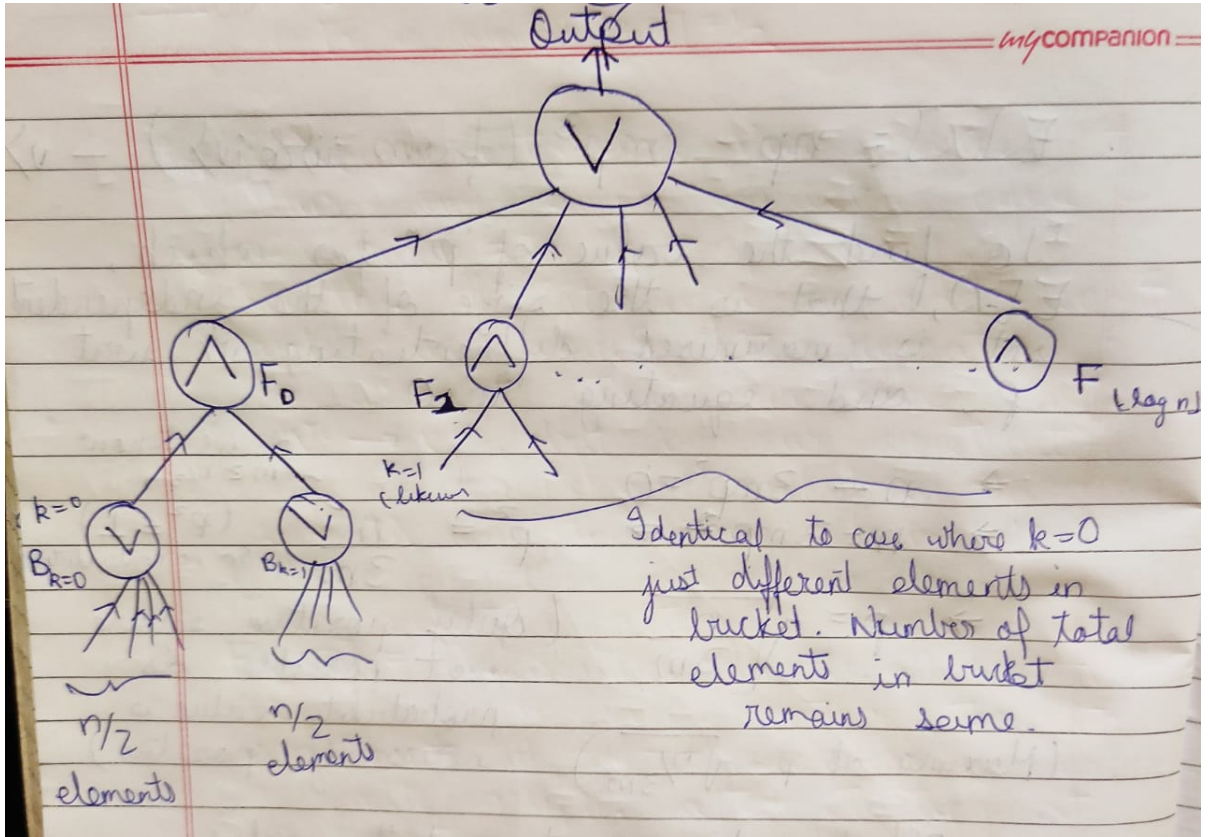


Figure 1: The circuit. Note: For  $n = 2^k$  we would have exact  $n/2$  elements in each bucket. Otherwise it would be at-most  $n/2$ , some buckets might have fewer, but as we are concerned about the asymptotic complexity finally, I'll proceed with the equality.

to each  $F$ , to take the outputs of the 2 OR gates corresponding to each bucket a level below as input to the AND) + ( $\log n$  wires to the one topmost OR gate to combine the results of all  $\log n$  AND gates corresponding to each  $F$ )

$$\begin{aligned}
 \text{Wires} &= 2 \times \frac{n}{2} \times \log n + 2 \log n + \log n \\
 &= n \log n + 3 \log n \\
 &= \boxed{O(n \cdot \log n)}
 \end{aligned}$$

**Fan-In: Unbounded.** As increase in the number of inputs for lowermost OR gates. As for increase in  $n$ , the number of elements in each bucket increases thus the number of inputs increase. Thus there is a gate with non-constant number of inputs.